 


Q1:

a)



```

module SR_2_input (input S, R, output Q, QB);
    nand #8 (Q, S, QB);
    nand #8 (QB, R, Q);
endmodule

module SR_3_input (input S, PS, R, PR, output Q, QB);

    nand #12 (Q, PS, S, QB);
    nand #12 (QB, PR, R, Q);

endmodule


```

b)

2_input_nand delay = 8ns.


3_input_nand delay = 12ns.

c)

 

Q2:

a)

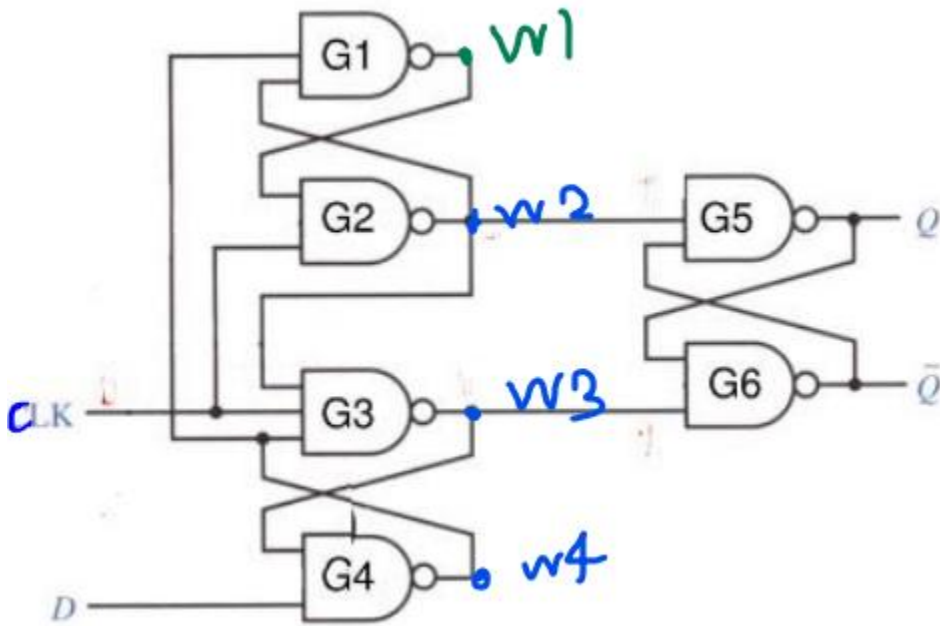

System Verilog code:

```
module SR_2_input (input S, R, output Q, QB);
    nand #8 (Q, S, QB);
    nand #8 (QB, R, Q);
endmodule

module SR_3_input (input S, PS, R, PR, output Q, QB);
    nand #12 (Q, PS, S, QB);
    nand #12 (QB, PR, R, Q);
endmodule

module D_flip_flop (input D, clk, output Q, QB);
    wire w1, w2, w3, w4;

    SR_2_input L1 (w4, clk, w1, w2);
    SR_3_input L2 (w2, clk, D, 1'b1, w3, w4);
    SR_2_input L3 (w2, w3, Q, QB);
endmodule
```

testbench:

```
module tb_b_q2 ();
    `timescale 1ns/1ns


    logic D, clk;
    wire Q, QB;

    D_flip_flop my_ff(D, clk, Q, QB);

    initial {D, clk} = 2'b00;

    initial repeat (30) #100 clk = ~clk;
    // initial repeat (20) #98 D = ~D;

     initial begin
        #100
        repeat (20) #60 D = ~D;
        #80 D = ~D;
        #40 D = ~D;
    end
endmodule
```



It works correctly unless we have a T_{setup} or hold violation, which the output in these situations should be unknown or X, BUT since we have simulation limit for our modelsim, it wont work correctly if we don't respect T_{Setup} & T_{hold} time.

And that's why we can see f.e 1 on the output at 700ps.

C & d)

T_{setup} : Before the riseedge of the clk:

we have to stop transitions of G4 gates inputs (D & clk), And let the nand gate propagate its value on its output.

so the delay for this beautiful patience will be equal to G4s delay.

nand_3_input delay= 12ns.

T_{Hold} : After the riseedge of the clk:



clk is an input for SR_latch (G3, G4), so just like D input we will have...

To stop transitions of G3 gates inputs (clk) , And let the nand gate propagate its value on its output.

And since we know we wont have clk transition in our circuit, we have to make D stop its transitions and wait until G3 propagate its value. because if we let D changes its value, the output of G4 wont be available for G3 input.


so the delay for this beautiful patience will be equal to G3s delay.

nand_3_input delay= 12ns.

 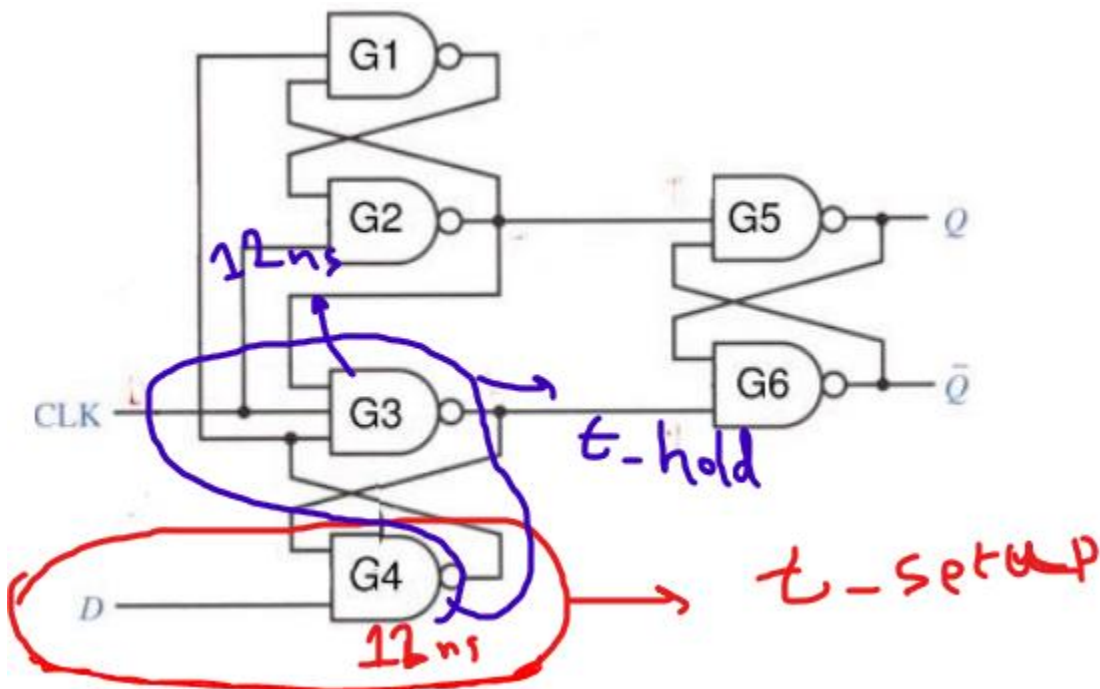

Q3:

e)

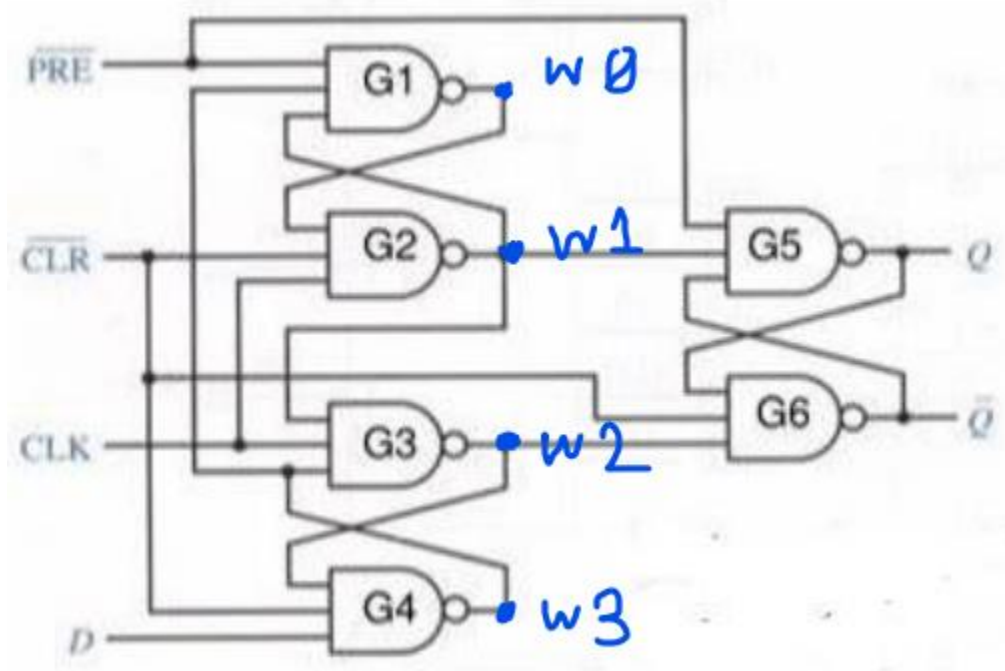

Here is the system Verilog code:

```
module SR_2_input (input S, R, output Q, QB);
    nand #8 (Q, S, QB);
    nand #8 (QB, R, Q);
endmodule

module SR_3_input (input S, PS, R, PR, output Q, QB);

    nand #12 (Q, PS, S, QB);
    nand #12 (QB, PR, R, Q);

endmodule

module D_flip_flop_PR (input D, clk, PRE, CLR, output Q, QB);

    wire wi[3:0];

    SR_3_input L1 (wi[3], ~ PRE, clk, ~ CLR, wi[0], wi[1]);
    SR_3_input L2 (wi[1], clk, D, ~CLR, wi[2], wi[3]);
    SR_3_input L3 (wi[1], ~ PRE, wi[2], ~ CLR, Q, QB);

endmodule
```

The T_Setup & T_Hold delays for this circuit are equal to G3 & G4 NAND gates:

T_Setup = 12ns.

T_Hold = 12ns.

f)

testbench without PRE & CLR transition:

```
module tb_q3_b ();
    `timescale 1ns/1ns

    logic D, clk, PRE, CLR;
    wire Q, QB;

    D_flip_flop_PR my_ff(D, clk, PRE, CLR, Q, QB);

    initial {D, clk, PRE, CLR} = 4'b0;

    initial repeat (15) #100 clk = ~clk;
    // initial repeat (20) #98 D = ~D;

    initial begin
        #100
        repeat (20) #60 D = ~D;
        #80 D = ~D;
        #40 D = ~D;
    end
endmodule
```

testbench with PRE transition:

```
module tb_q3_g ();
    `timescale 1ns/1ns

    logic D, clk, PRE, CLR;
    wire Q, QB;


    D_flip_flop_PR my_ff(D, clk, PRE, CLR, Q, QB);

    initial {D, clk, PRE, CLR} = 4'b0;


    initial repeat (15) #100 clk = ~clk;

    initial begin
        #100
        repeat (20) #60 D = ~D;
        #80 D = ~D;
        #40 D = ~D;
    end
    initial begin
        #450 PRE = ~ PRE;
        #100 PRE = ~ PRE;
    end
endmodule
```

 
Waveform without PRE & CLR transition (which has wrong outputs in some points (f.e 500ps & 700ps) because of T_setup&hold violations like Q2).



 Waveform with PRE transition:
as we can see on (450ps till 550) PRE has priority over clk.



 Waveform with CLR transition:
as we can see on (250ps till 350) CLR has priority over clk too.



Waveform with both CLR & PRE transition:
if we active both of them at the same time, the memory will be gone.

